

Topic 4 · Electricity and magnetism

Magnetism, charge and current, circuit calculations, electrical safety in the home, the motor effect, induction and transformers.

SUGGESTED TIME	TOTAL MARKS	QUESTIONS	MULTIPLE CHOICE
50 minutes	41	10	6

SECTION	4 · Electricity and magnetism
IN THE FORMAT OF	Papers 1 and 2 (multiple choice), Papers 3 and 4 (theory), Paper 6 (alternative to practical)
ROUTES	Core only — 5 questions, 19 marks. Core and Supp. — the whole paper, 10 questions, 41 marks. Every question is tagged in the left margin.
DEMAND	Recall 2 · Routine 4 · Demanding 3 · Discriminating 1 <i>Pitched at the board's own level, not above it. Multiple choice is mostly one step, with a couple of two-step items and one that rewards the candidate who does not take the obvious route. Structured questions open on a 1-mark recall and close on an explanation or a suggestion worth two marks — the marks real candidates most often drop.</i>
SYLLABUS POINTS	4.1 · 4.2 · 4.3 · 4.4 · 4.5

INSTRUCTIONS

- Answer all questions in the spaces provided.
- Show your working. Method marks are awarded even where the final answer is wrong.
- Give your answers to a sensible number of significant figures, with a unit.
- The mark scheme for this paper follows the last question.

Written by GioPhysics from the published syllabus. These are practice papers in the style of Cambridge IGCSE Physics 0625; they are not Cambridge papers, contain no past-paper questions, and the official syllabus and specimen materials remain the authority.

Cambridge IGCSE Physics 0625 syllabus — <https://www.cambridgeinternational.org/Images/697209-2026-2028-syllabus.pdf>

Topic 4 · Electricity and magnetism

Answer all questions. 41 marks in 50 minutes.

1

CORE

MULTIPLE CHOICE · RECALL · 4.1

[1]

Which statement about a permanent magnet and a piece of unmagnetised iron is correct?

- A** The magnet attracts the iron, and the iron attracts the magnet.
- B** The magnet attracts the iron, but the iron has no effect on the magnet.
- C** The magnet repels the iron if the south pole is brought close.
- D** The iron must first be magnetised before any force acts.

Answer

2

SUPP.

MULTIPLE CHOICE · ROUTINE · 4.2

[1]

A current of 250 mA flows in a lamp for 4.0 minutes. How much charge passes through the lamp?

- A** 1.0 C
- B** 60 C
- C** 1000 C
- D** 60 000 C

Answer

3

SUPP.

MULTIPLE CHOICE · ROUTINE · 4.3

[1]

Two resistors of $6.0\ \Omega$ and $3.0\ \Omega$ are connected in parallel. What is their combined resistance?

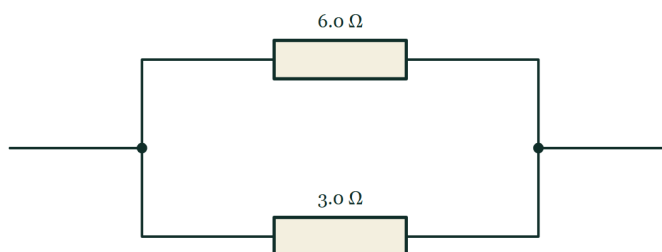


Fig. 3.1 A circuit diagram of two resistors connected side by side between the same pair of points. A wire arrives from the left and reaches a junction, marked with a dot, where it divides into two branches. The upper branch contains a resistor labelled $6.0\ \text{ohm}$ and the lower branch a resistor labelled $3.0\ \text{ohm}$. The two branches rejoin at a second junction dot on the right, from which a single wire continues away to the right.

- A $0.50\ \Omega$
- B $2.0\ \Omega$
- C $4.5\ \Omega$
- D $9.0\ \Omega$

Answer

4

CORE

MULTIPLE CHOICE · DEMANDING · 4.4

[1]

An electric heater is rated at $230\ \text{V}$, $2.0\ \text{kW}$. Fuses of $3\ \text{A}$, $5\ \text{A}$, $10\ \text{A}$ and $13\ \text{A}$ are available. Which is the most suitable fuse for the heater?

- A $3\ \text{A}$
- B $5\ \text{A}$
- C $10\ \text{A}$
- D $13\ \text{A}$

Answer

A straight wire carrying a current is placed at right angles to a magnetic field. In which direction does the force on the wire act?

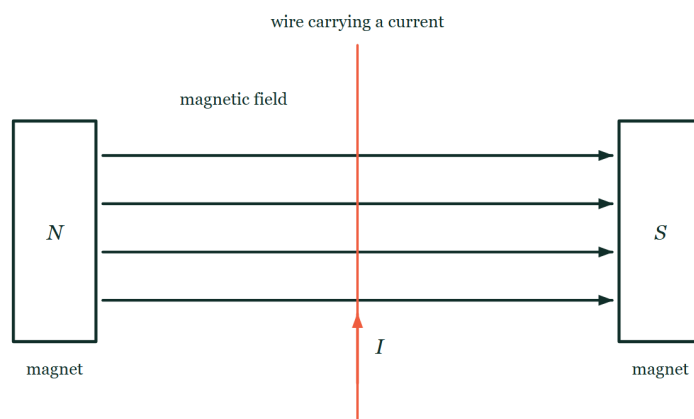


Fig. 5.1 Two magnets face each other across a gap, the left one presenting its north pole and the right one its south pole, with the flat pole faces vertical and parallel. Four horizontal arrows drawn across the gap from the north pole to the south pole represent the magnetic field. A straight wire runs vertically down the page through the middle of the gap, so that it crosses the field lines at right angles, and a short arrow on the wire labelled I shows the current flowing up the page.

- A** along the wire, in the direction of the current
- B** along the magnetic field lines
- C** at right angles to both the current and the field
- D** there is no force unless the wire moves

Answer

A transformer has 200 turns on the primary coil and 5000 turns on the secondary coil. The primary is connected to a 12 V a.c. supply. What is the output voltage?

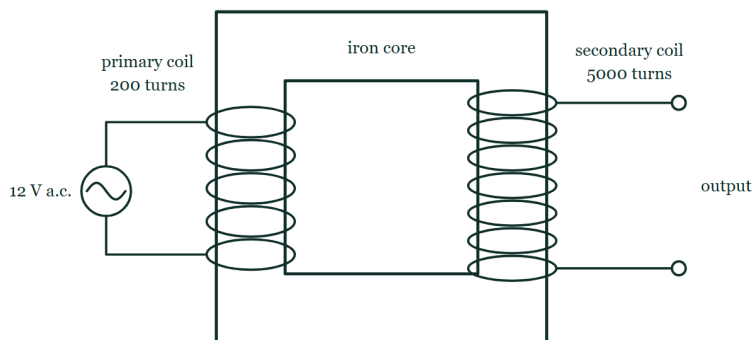


Fig. 6.1 A transformer drawn as a rectangular iron core with a hollow centre. Wound around the left limb is the primary coil, labelled 200 turns and drawn as five loops encircling the limb; its two ends run out to the left to a 12 V a.c. supply, drawn as a circle containing one cycle of a sine wave. Wound around the right limb is the secondary coil, labelled 5000 turns and drawn as seven closer-spaced loops; its two ends run out to the right to a pair of open output terminals.

- A 0.48 V
- B 12 V
- C 300 V
- D 1200 V

Answer

A 12 V battery of negligible internal resistance is connected to a 40 Ω resistor in series with a parallel combination of a 30 Ω resistor and a 60 Ω resistor.

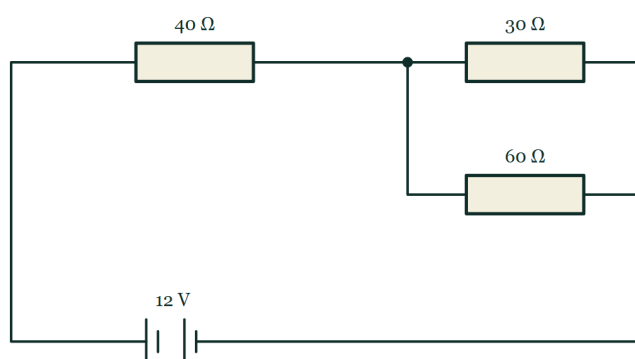


Fig. 7.1 Circuit diagram. From the positive terminal of the 12 V battery, drawn at the foot of the circuit with its long plate on the left, the wire runs round to a resistor labelled 40 ohm. Beyond that resistor the circuit reaches a junction and divides into two parallel branches, the upper one containing a resistor labelled 30 ohm and the lower one a resistor labelled 60 ohm. The branches rejoin at a second junction, and a single wire returns from there to the negative terminal of the battery.

- (a) **CALCULATE** [2]
Calculate the combined resistance of the parallel pair.
.....
.....
- (b) **CALCULATE** [2]
Calculate the current drawn from the battery.
.....
.....
- (c) **DETERMINE** [2]
Determine the potential difference across the parallel pair.
.....
.....
- (d) **DETERMINE** [2]
Determine the current in the $60\ \Omega$ resistor.
.....
.....
- (e) **EXPLAIN** [2]
The $60\ \Omega$ resistor is now removed from the circuit, leaving a break in that branch.
Explain what happens to the current drawn from the battery.
.....
.....
.....
-

A bar magnet is pushed, north pole first, into a coil of insulated wire connected to a sensitive centre-zero ammeter. The ammeter needle deflects to the right while the magnet is moving in.

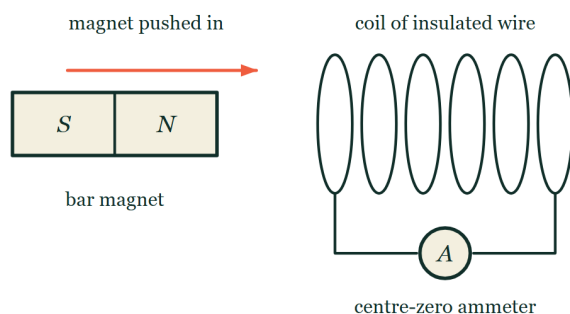


Fig. 8.1 A bar magnet lies to the left of a coil of insulated wire, on the same horizontal axis as the coil. The magnet's south pole is at its left-hand end and its north pole at the right-hand end, so the north pole faces the coil. An arrow above the magnet points towards the coil, showing the direction in which the magnet is pushed. The coil is drawn as six loops, and wires from its two ends run down and join a centre-zero ammeter, whose face is shown as a circle marked A with no needle drawn on it.

(a) STATE

[1]

State what happens to the ammeter reading while the magnet is held stationary inside the coil.

.....

(b) EXPLAIN

[3]

Explain, in terms of magnetic field lines, why a current is produced only while the magnet is moving.

.....

(c) STATE

[2]

State two changes to the experiment that would each increase the size of the deflection.

.....

(d) EXPLAIN

[3]

The magnet is now pulled out of the coil, south pole first, at the same speed. Explain what is observed on the ammeter, and why.

.....

A household electric shower is connected to the 230 V mains supply through a fuse and an earth wire. The shower has a metal case and is marked 8.5 kW.

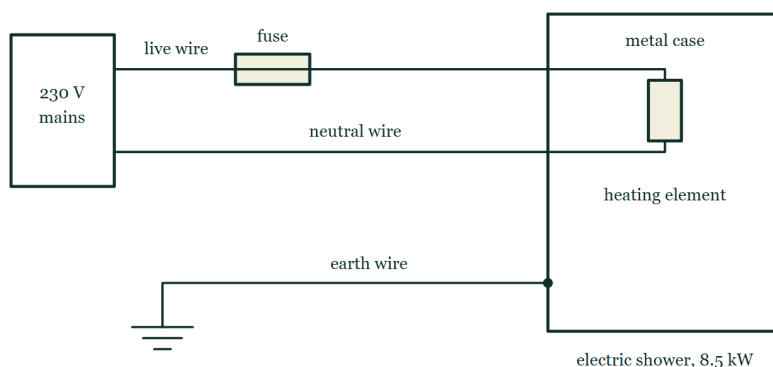


Fig. 9.1 A wiring diagram of the electric shower. A box on the left marked 230 V mains has two wires leaving it: the live wire, which passes through a fuse drawn as a small rectangle with a line through it, and the neutral wire, which runs straight across. Both enter the outline of the shower, where they are joined to each other by the heating element. The shower's outline is labelled metal case and the appliance is marked 8.5 kW. A third wire, the earth wire, runs from an earth symbol of three shortening horizontal bars across to the metal case, meeting it at a solid connecting dot.

(a) **CALCULATE**

[2]

Calculate the current in the shower when it is operating normally.

.....

.....

(b) **EXPLAIN**

[3]

Explain how the earth wire and the fuse together protect a person who touches the metal case if a live wire comes loose inside the shower.

.....

.....

.....

(c) **CALCULATE**

[3]

The shower is used for a total of 30 minutes each day. Electrical energy costs 24 cents per kilowatt-hour. Calculate the cost of using the shower for 30 days.

.....

.....

.....

A student investigates how the current in a filament lamp depends on the potential difference across it. She connects the lamp to a variable power supply, with an ammeter in series and a voltmeter across the lamp.

The student's results

V / V	0.0	1.0	2.0	3.0	4.0	5.0	6.0
I / A	0.00	0.17	0.28	0.36	0.42	0.47	0.51

(a) **STATE**

[2]

State how the ammeter and the voltmeter must each be connected in the circuit.

.....

.....

(b) **DETERMINE**

[3]

Determine the resistance of the lamp when the potential difference across it is 1.0 V, and again when it is 6.0 V.

.....

.....

.....

.....

(c) **EXPLAIN**

[3]

Explain, in terms of the filament, why the resistance changes in the way your answers to (b) show.

.....

.....

.....

.....

Topic 4 · Electricity and magnetism — mark scheme

One line per mark, as an examiner would award them. A note under a part is the error that part is set to catch.

1 CORE	MULTIPLE CHOICE · RECALL · 4.1	[1]
	Which statement about a permanent magnet and a piece of unmagnetised iron is correct?	
	KEY A The magnet attracts the iron, and the iron attracts the magnet.	
	<i>C is the item's real target: an unmagnetised magnetic material is always attracted, whichever pole approaches. Repulsion is the only sure test for a magnet.</i>	
		A01
2 SUPP.	MULTIPLE CHOICE · ROUTINE · 4.2	[1]
	A current of 250 mA flows in a lamp for 4.0 minutes. How much charge passes through the lamp?	
	KEY B 60 C	
	<i>A converts the minutes but not the milliamps. C converts the milliamps but not the minutes. Both unit conversions have to be done, which is the point of the item.</i>	
		A02
3 SUPP.	MULTIPLE CHOICE · ROUTINE · 4.3	[1]
	Two resistors of 6.0 Ω and 3.0 Ω are connected in parallel. What is their combined resistance?	
	KEY B 2.0 Ω	
	<i>D is the series total and C is the mean — both offered to candidates who reach for an average. A stops at 1/R without inverting. Any parallel answer must be smaller than the smaller resistor, which rules out C and D at a glance.</i>	
		A02
4 CORE	MULTIPLE CHOICE · DEMANDING · 4.4	[1]
	An electric heater is rated at 230 V, 2.0 kW. Fuses of 3 A, 5 A, 10 A and 13 A are available. Which is the most suitable fuse for the heater?	
	KEY C 10 A	
	<i>The working current is $2000 / 230 = 8.7$ A, so the fuse must be the smallest standard rating above it. A and B are below the working current and would melt every time the heater was switched on. D would carry the working current safely but is so far above it that a fault current of 12 A — enough to overheat the flex — would flow without ever blowing the fuse.</i>	
		A02
5 CORE	MULTIPLE CHOICE · RECALL · 4.5	[1]
	A straight wire carrying a current is placed at right angles to a magnetic field. In which direction does the force on the wire act?	
	KEY C at right angles to both the current and the field	
	<i>D confuses the motor effect with electromagnetic induction — a current-carrying wire in a field experiences a force whether or not it is moving.</i>	
		A01

6

SUPP.

MULTIPLE CHOICE · ROUTINE · 4.5

[1]

A transformer has 200 turns on the primary coil and 5000 turns on the secondary coil. The primary is connected to a 12 V a.c. supply. What is the output voltage?

KEY **C 300 V**

A inverts the turns ratio. With more turns on the secondary this is a step-up transformer, so any answer at or below 12 V can be discarded before the arithmetic.

A02

7

SUPP.

STRUCTURED · DEMANDING · 4.2 · 4.3

[10]

A 12 V battery of negligible internal resistance is connected to a 40 Ω resistor in series with a parallel combination of a 30 Ω resistor and a 60 Ω resistor.

(a) CALCULATE · A02

[2]

Calculate the combined resistance of the parallel pair.

1 $1/R = 1/30 + 1/60 = 3/60$

2 $R = 20 \Omega$

(b) CALCULATE · A02

[2]

Calculate the current drawn from the battery.

1 total resistance = $40 + 20 = 60 \Omega$

2 $I = V / R = 12 / 60 = 0.20 \text{ A}$

(c) DETERMINE · A02

[2]

Determine the potential difference across the parallel pair.

1 p.d. across the 40 Ω resistor = $0.20 \times 40 = 8.0 \text{ V}$

2 p.d. across the pair = $12 - 8.0 = 4.0 \text{ V}$ (or $0.20 \times 20 = 4.0 \text{ V}$)

(d) DETERMINE · A02

[2]

Determine the current in the 60 Ω resistor.

1 $I = V / R = 4.0 / 60$

2 $I = 0.067 \text{ A}$ (67 mA)

(e) EXPLAIN · A02

[2]

The 60 Ω resistor is now removed from the circuit, leaving a break in that branch. Explain what happens to the current drawn from the battery.

1 the total resistance increases, because the parallel pair is replaced by the 30 Ω resistor alone, giving 70 Ω instead of 60 Ω

2 so the current from the battery decreases (to about 0.17 A)

Candidates routinely say removing a resistor lowers the resistance. Removing one branch of a parallel pair raises it, and this part is set precisely on that.

8 SUPP.	STRUCTURED · DISCRIMINATING · 4.5	[9]
	A bar magnet is pushed, north pole first, into a coil of insulated wire connected to a sensitive centre-zero ammeter. The ammeter needle deflects to the right while the magnet is moving in.	
(a)	STATE · A01 State what happens to the ammeter reading while the magnet is held stationary inside the coil. 1 the reading returns to (and stays at) zero	[1]
(b)	EXPLAIN · A01 Explain, in terms of magnetic field lines, why a current is produced only while the magnet is moving. 1 an e.m.f. is induced when the magnetic field lines linking the coil change 2 moving the magnet changes the number of field lines through the coil, cutting the turns of wire 3 a stationary magnet gives an unchanging field through the coil, so no e.m.f. and no current	[3]
(c)	STATE · A01 State two changes to the experiment that would each increase the size of the deflection. 1 move the magnet faster 2 any one of: use a stronger magnet; use a coil with more turns; use a coil of smaller cross-sectional area wound closer to the magnet	[2]
(d)	EXPLAIN · A02 The magnet is now pulled out of the coil, south pole first, at the same speed. Explain what is observed on the ammeter, and why. 1 the needle deflects to the left — the current is in the opposite direction 2 because the field through the coil is changing in the opposite sense as the magnet is withdrawn 3 the size of the deflection is the same, because the rate of change of the field is the same <i>Three marks and three separate ideas: direction, cause and size. Most answers get the reversal and stop, and stop at one mark.</i>	[3]

9 CORE	STRUCTURED · ROUTINE · 4.4	[8]
	A household electric shower is connected to the 230 V mains supply through a fuse and an earth wire. The shower has a metal case and is marked 8.5 kW.	
	(a) CALCULATE · A02 Calculate the current in the shower when it is operating normally. 1 $I = P / V = 8500 / 230$ 2 $I = 37 \text{ A}$	[2]
	(b) EXPLAIN · A01 Explain how the earth wire and the fuse together protect a person who touches the metal case if a live wire comes loose inside the shower. 1 the earth wire connects the metal case to earth through a very low resistance path 2 if the live wire touches the case, a very large current flows to earth rather than through the person 3 this current melts the fuse, breaking the live wire and isolating the appliance <i>The fuse must be described as being in the live wire. A fuse in the neutral would blow but leave the case live, and mark schemes withhold the mark for exactly that reason.</i>	[3]
	(c) CALCULATE · A02 The shower is used for a total of 30 minutes each day. Electrical energy costs 24 cents per kilowatt-hour. Calculate the cost of using the shower for 30 days. 1 energy per day = $8.5 \text{ kW} \times 0.50 \text{ h} = 4.25 \text{ kWh}$ 2 energy in 30 days = 127.5 kWh 3 cost = $127.5 \times 24 = 3060 \text{ cents} = \\30.60	[3]
10 CORE	PRACTICAL SKILLS · DEMANDING · 4.3	[8]
	A student investigates how the current in a filament lamp depends on the potential difference across it. She connects the lamp to a variable power supply, with an ammeter in series and a voltmeter across the lamp.	
	(a) STATE · A03 State how the ammeter and the voltmeter must each be connected in the circuit. 1 the ammeter is connected in series with the lamp 2 the voltmeter is connected in parallel with (across) the lamp	[2]
	(b) DETERMINE · A02 Determine the resistance of the lamp when the potential difference across it is 1.0 V, and again when it is 6.0 V. 1 $R = V / I$ used at both points 2 at 1.0 V: $R = 1.0 / 0.17 = 5.9 \Omega$ 3 at 6.0 V: $R = 6.0 / 0.51 = 11.8 \Omega$ (accept 12 Ω)	[3]
	(c) EXPLAIN · A02 Explain, in terms of the filament, why the resistance changes in the way your answers to (b) show. 1 as the current increases the filament gets hotter 2 the metal ions in the filament vibrate with greater amplitude 3 so the electrons collide with them more often and the resistance increases <i>A graph of I against V for a filament lamp curves towards the V axis. Candidates who say the lamp "does not obey Ohm's law" have named the observation, not explained it, and the marks here are for the mechanism.</i>	[3]

What the command words are asking for

Every board publishes these and marks to them. A candidate who explains where the question said state has spent four minutes earning one mark; one who states where it said explain has earned none.

Calculate	Work out from given facts, figures or information.
Define	Give the precise meaning.
Describe	State the points of a topic; give characteristics and main features.
Determine	Establish an answer using the information available.
Estimate	Suggest an approximate value.
Explain	Set out purposes or reasons; make relationships evident; give why and/or how.
Give	Produce an answer from a given source or recall.
Identify	Name, select or recognise.
Show (that)	Provide structured evidence that leads to a given result.
State	Express in clear terms.
Suggest	Apply knowledge and understanding to situations where there is a range of valid responses in order to make proposals.

WHAT IS BEING TESTED

IGCSE assessment objectives

Every candidate sits two theory papers and one practical-skills paper. Core takes Papers 1 and 3 and is capped at grade C; Extended takes Papers 2 and 4 and reaches A*. Both then take either Paper 5 (practical test) or Paper 6 (alternative to practical), which carries 20% either way. Theory papers give you no formula sheet.

A01

11 MARKS · 27%
QUALIFICATION 50%

Knowledge with understanding

Recall, describe, explain and use physics ideas, terminology, instruments and conventions.

A02

28 MARKS · 68%
QUALIFICATION 30%

Handling information and problem-solving

Locate and interpret information, translate between forms, calculate, reason, and apply physics to unfamiliar situations.

A03

2 MARKS · 5%
QUALIFICATION 20%

Experimental skills and investigations

Plan, use apparatus, record and present observations, analyse, evaluate, and suggest improvements.

Written by GioPhysics from the published syllabus. These are practice papers in the style of Cambridge IGCSE Physics 0625; they are not Cambridge papers, contain no past-paper questions, and the official syllabus and specimen materials remain the authority.

Cambridge IGCSE Physics 0625 syllabus — <https://www.cambridgeinternational.org/Images/697209-2026-2028-syllabus.pdf>